QI:

A $100 + j150-\Omega$ load is connected to a 75- Ω lossless line. Find:

- (a) Γ
- (b) s
- (c) The load admittance Y_L
- (d) Z_{in} at 0.4 λ from the load
- (e) The locations of $V_{\rm max}$ and $V_{\rm min}$ with respect to the load if the line is 0.6 λ long
- (f) Z_{in} at the generator.

QZ

With an unknown load connected to a slotted air line, s=2 is recorded by a standing wave indicator and minima are found at 11 cm, 19 cm, . . . on the scale. When the load is replaced by a short circuit, the minima are at 16 cm, 24 cm, If $Z_0=50~\Omega$, calculate λ , f, and Z_L .

[Solution #1]

(a) We can use the Smith chart to solve this problem. The normalized load impedance is

$$z_L = \frac{Z_L}{Z_0} = \frac{100 + j150}{75} = 1.33 + j2$$

We locate this at point P on the Smith chart of Figure 11.16. At P, we obtain

$$|\Gamma_L| = \frac{OP}{OQ} = \frac{6 \text{ cm}}{9.1 \text{ cm}} = 0.659$$

 $\theta_L = \text{angle } POS = 40^\circ$

(b) Draw the constant circle passing through P and obtain

$$|\mathcal{I}| \qquad s = 4.82$$

Check:

$$s = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.659}{1 - 0.659} = 4.865$$

(c) To obtain Y_L , extend PO to POP' and note point P' where the constant f-circle meets POP'. At P', obtain

$$y_L = 0.228 - j0.35$$

The load admittance is

$$Y_L = Y_0 y_L = \frac{1}{75} (0.228 - j0.35) = 3.04 - j4.67 \text{ m}$$

Check:

$$Y_L = \frac{1}{Z_L} = \frac{1}{100 + j150} = 3.07 - j4.62 \text{ mV}$$
 (720 = 41T)

(d) 0.4λ corresponds to an angular movement of $0.4 \times 720^{\circ} = 288^{\circ}$ on the constant s-circle. From P, we move 288° toward the generator (clockwise) on the Infection to reach point R. At R,

$$z_{\rm in} = 0.3 + j0.63$$

Hence

$$Z_{\text{in}} = Z_{\text{o}} z_{\text{in}} = 75 (0.3 + j0.63)$$

= 22.5 + j47.25 \Omega

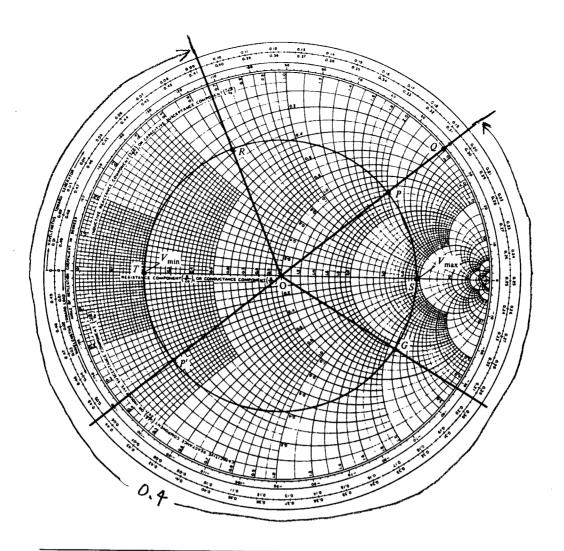


Figure 11.16 For Example 11.5.

Hence,

 Γ_{L} = 0.659 $\underline{/40^{\circ}}$

Check:

$$\Gamma_{L} = \frac{Z_{L} - Z_{0}}{Z_{L} + Z_{0}} = \frac{100 + j150 - 75}{100 + j150 + 75}$$
$$= 0.659 /40^{\circ}$$

Check:

$$\beta \ell = \frac{2\pi}{\lambda} (0.4\lambda) = 360^{\circ} (0.4) = 144^{\circ}$$

$$Z_{\text{in}} = Z_{\text{o}} \left[\frac{Z_L + jZ_{\text{o}} \tan \beta \ell}{Z_{\text{o}} + jZ_L \tan \beta \ell} \right]$$

$$= \frac{75 (100 + j150 + j75 \tan 144^{\circ})}{[75 + j(100 + j150) \tan 144^{\circ}]}$$

$$= 54.41 / 65.25^{\circ}$$

or

$$Z_{in} = 21.9 + j47.6 \,\mathrm{U}$$

(e) 0.6\(\lambda\) corresponds to an angular movement of

$$0.6 \times 720^{\circ} = 432^{\circ} = 1 \text{ revolution} + 72^{\circ}$$

Thus, we start from P (load end), move along the C-circle 432°, or one revolution plus 72°, and reach the generator at point G. Note that to reach G from P, we have passed through point T (location of V_{\min}) once and point S (location of V_{\max}) twice. Thus, from the load,

1st
$$V_{\text{max}}$$
 is located at $\frac{40^{\circ}}{720^{\circ}} \lambda = 0.055\lambda$

2nd
$$V_{\text{max}}$$
 is located at $0.0555\lambda + \frac{\lambda}{2} = 0.555\lambda$

and the only V_{\min} is located at $0.055\lambda + \lambda/4 = 0.3055\lambda$

(f) At G (generator end),

$$z_{in} = 1.8 - j2.2$$

$$Z_{\rm in} = 75(1.8 - j2.2) = 135 - j165 \,\Omega.$$


This can be checked by using eq. (11.34), where
$$\beta \ell = \frac{2\pi}{\lambda}$$
 (0.6 λ) = 216°.

We can see how much time and effort is saved using the Smith chart.

Consider the standing wave patterns as in Figure 11.23(a). From this, we observe that

$$\frac{\lambda}{2} = 19 - 11 = 8 \text{ cm}$$
 or $\lambda = 16 \text{ cm}$
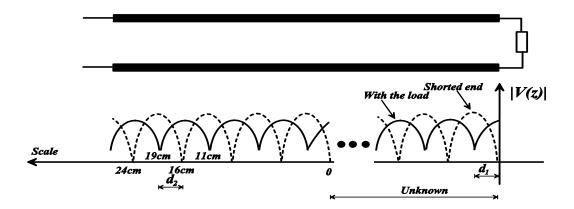
$$f = \frac{u}{\lambda} = \frac{3 \times 10^8}{16 \times 10^{-2}} = 1.875 \text{ GHz}$$



From the above figure, we can see that the distance of $|V|_{min}$ with the load, d_1 , is equal to d_2 . That is,

$$d_1 = d_2 = 19cm - 16cm = 3cm$$
.

Since s=2 (i.e. VSWR=2), we can locate point P: z=r=s=2.0 (which is also the $|V|_{max}$ point). Then draw the constant- $|\Gamma|$ circle and find the $|V|_{min}$ point.

By moving from the $|V|_{min}$ point towards the load by a distance of 3cm/16cm=0.1875, we can read:

$$\begin{split} \tilde{Z}_L &= 1.38 - j0.80 \\ Z_L &= 50(1.38 - j0.80) = 69 - j40 \; (\Omega) \end{split}$$

