ECED 4301 Assignment #7 Solution

$$\delta = \frac{1}{\sqrt{\pi f \,\mu_c \sigma_c}} = \frac{1}{\sqrt{\pi x 80 x 10^6 x 4 \pi x 10^{-7} x 5.28 x 10^7}} = 7.744 x 10^{-6}$$

$$R = \frac{1}{2\pi\delta\sigma_c} \left[\frac{1}{a} + \frac{1}{b} \right] = \frac{\left[\frac{1}{0.8x10^{-3}} + \frac{1}{2.6x10^{-3}} \right]}{2\pi x7.744x10^{-6} x5.28x10^7} = \frac{10^3 (1.25 + 0.3836)}{2569.09} = \underline{0.6359 \text{ G}}$$

$$L = \frac{\mu}{2\pi} \ln \frac{b}{a} = \frac{4\pi x 10^{-7}}{2\pi} \ln \frac{2.6}{0.8} = \underline{2.357 x 10^{-7} \text{ H/m}}$$

$$G = \frac{2\pi\sigma}{\ln\frac{b}{a}} = \frac{2\pi x 10^{-5}}{\ln\frac{2.6}{0.8}} = \underline{5.33x10^{-5} \text{ S/m}}$$

$$C = \frac{2\pi\varepsilon}{\ln\frac{b}{a}} = \frac{2\pi x 3.5 x \frac{10^{-9}}{36\pi}}{\ln\frac{2.6}{0.8}} = \underline{1.65 x 10^{-10} \text{ F/m}}$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$Z_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\gamma Z_o = R + j\omega L = (0.01 + j4)(50 + j0) = 0.5 + j200$$

$$R = 0.5 \Omega/m$$

$$L = \frac{200}{\omega} = \frac{200}{2\pi x 800 x 10^6} = \frac{3.979 x 10^{-8} \text{ H/m}}{200 x 10^{-8} \text{ H/m}}$$

$$\frac{\gamma}{Z_o} = G + j\omega C = \frac{(0.01 + j4)}{50}$$

$$G = \frac{0.01}{50} = \frac{2x10^{-4} \text{ S/m}}{50x2\pi x800x10^6}$$

$$C = \frac{4}{50\omega} = \frac{4}{50x2\pi x800x10^6} = \frac{1.591x10^{-11} \text{ F/m}}{1.591x10^{-11}}$$

(a)
$$R + j\omega L = 40 + j2\pi \times 10^7 \times 0.2 \times 10^{-6} = 41.93 \angle 17.44^\circ$$

$$G + j\omega C = 400 \times 10^{-6} + j2\pi \times 10^{7} \times 0.5 \times 10^{-9} = 3.142 \times 10^{-2} \angle 89.27^{\circ}$$

$$Z_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \underbrace{29.59 - j21.43 \,\Omega}_{}$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega L)} = 0.685 + j0.921 = \alpha + j\beta$$

$$u = \frac{\omega}{\beta} = \frac{2\pi \times 10^7}{0.921} = \underline{6.823 \times 10^7 \text{ m/s}}$$

(b)
$$\alpha = 0.685 \text{ Np/m} = 0.685 \times 8.686 \text{ dB/m} = 5.95 \text{ dB/m}$$

$$\alpha l = 30 \rightarrow l = \frac{30}{5.95} = \frac{5.042 \text{ m}}{}$$

(a)
$$\alpha = \underline{0.0025 \text{ Np/m}}, \quad \beta = \underline{2 \text{ rad/m}},$$

$$u = \frac{\omega}{\beta} = \frac{10^8}{2} = \frac{5 \times 10^7 \text{ m/s}}{2}$$

(b)
$$\Gamma = \frac{V_o}{V_o^+} = \frac{60}{120} = \frac{1}{2}$$

But
$$\Gamma = \frac{Z_L - Z_o}{Z_L + Z_o} \to \frac{1}{2} = \frac{300 - Z_o}{300 + Z_o} \to \underline{Z_o = 100\Omega}$$

$$I(l') = \frac{120}{Z_o} e^{0.0025l'} \cos(10^8 + 2l') - \frac{60}{Z_o} e^{-0.0025l'} \cos(10^8 t - 2l')$$
$$= 1.2e^{0.0025l'} \cos(10^8 + 2l') - 0.6e^{-0.0025l'} \cos(10^8 t - 2l') A$$

$$=1.2e^{0.0025l'}\cos(10^8+2l')-0.6e^{-0.0025l'}\cos(10^8t-2l')A$$

$$I_{l} = \frac{V_{L}}{Z_{L}}, \Gamma = \frac{Z_{L} - Z_{o}}{Z_{L} + Z_{o}} = \frac{50e^{j30^{o}} - 50}{50e^{j30^{o}} + 50}$$

$$\approx j0.2679$$

From eq.(11.30),

$$V_o^+ = \frac{1}{2} (V_L + Z_o \cdot \frac{V_L}{Z_L}) e^{it} = \frac{V_L}{2Z_L} (Z_L + Z_o) e^{it}$$

$$V_o^- = \frac{V_L}{2Z_L} (Z_L - Z_o) e^{-it}$$

Substituting these in eq.(11.25),

$$\begin{split} I_{s} &= \frac{V_{L}}{2Z_{L}Z_{o}} \Big[(Z_{L} + Z_{o})e^{\gamma l}e^{-\gamma z} - (Z_{L} - Z_{o})e^{-\gamma l}e^{\gamma z} \Big] \\ &= \frac{V_{L}/Z_{o}}{1 + \Gamma} \Big[e^{-\gamma(z-l)} - \Gamma e^{\gamma(z-l)} \Big] \end{split}$$

But
$$l-z=\frac{\lambda}{8}$$
 or $z-l=-\frac{\lambda}{8}$

$$I_{s} = \frac{10\angle 25^{\circ}}{1.035\angle 15^{\circ}} \left(\frac{1}{50}\right) \left(e^{j\frac{\pi}{4}} - j0.2679e^{-j\frac{\pi}{4}}\right)$$
$$= \underline{0.1414\angle 55^{\circ} A}$$

Using the Smith chart,
$$z_L = \frac{60 - j40}{75} = 0.8 - j0.533$$

 $l = \frac{3}{4}\lambda \longrightarrow \frac{3}{4}x720^\circ = 540^\circ$
At C, $Z_{in} = 75(0.8654 + j0.5769) = 65 + j43 \Omega$
 $z_{in} = \frac{65 + j43}{100} = 0.65 + j0.43$
 $\frac{\lambda}{2} \longrightarrow \frac{720^\circ}{2} = 360^\circ$
At B, $Z_{in} = 65 + j43$
 $z_{in} = \frac{65 + j43}{50} = 1.2981 + 0.8654$
 $\frac{\lambda}{4} \longrightarrow \frac{720^\circ}{4} = 180^\circ$
At A, $Z_{in} = 50(0.53 - j0.35) = \underline{26.7 - j17.8 \Omega}$

(a)
$$z_L = \frac{Z_L}{Z_o} = \frac{75 + j60}{50} = 1.5 + j1.2$$

 $|\Gamma| = \frac{OP}{OQ} = \frac{3.8 \text{cm}}{8 \text{cm}} = 0.475, \quad \theta_{\Gamma} = 42^{\circ}$
 $\Gamma = \underline{0.475 \angle 42^{\circ}}$


(Exact value = $0.4688 \angle 41.76^{\circ}$)

(b)
$$s=2.8$$
 (Exact value = 2.765)

(c)
$$0.2\lambda \to 0.2x720^{\circ} = 144^{\circ}$$

 $z_{in} = 0.55 - j0.65$
 $Z_{in} = Z_{o}z_{in} = 50(0.55 + j0.65) = 27.5 + j32.5 \Omega$

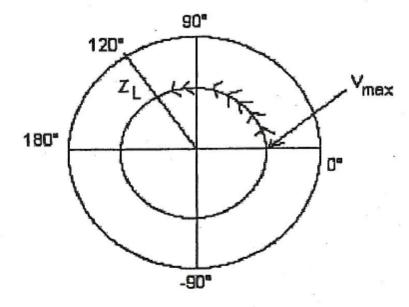- (d) Since $\theta_{\Gamma} = 42^{\circ}$, V_{min} occurs at $\frac{42}{720} \lambda = \underline{0.05833\lambda}$
- (e) same as in (d), i.e.. 0.05833λ



(a)
$$\frac{\lambda}{2} = 120cm \rightarrow \lambda = 2.4m$$

$$u = f\lambda \rightarrow f = \frac{u}{\lambda} = \frac{3 \times 10^8}{2.4} = \underline{125MHz}$$

(b)
$$40cm = \frac{40\lambda}{240} = \frac{\lambda}{6} \to \frac{720^{\circ}}{6} = 120^{\circ}$$

$$Z_L = Z_o z_L = 150(0.48 + j0.48)$$

= $\frac{72 + j72}{2} \Omega$

(Exact value = $73.308 + j70.324 \Omega$)

(c)
$$|\Gamma| = \frac{s-1}{s+1} = \frac{1.6}{3.9} = 0.444,$$

 $\Gamma = \underbrace{0.444 \angle 120^{\circ}}$

$$z_L = \frac{Z_L}{Z_o} = \frac{120 + j220}{50} = 2.4 + j4.4$$

We follow Example 11.7. At A, y_s=-j3 and at B admittance is

$$Y_s = Y_o y_s = \frac{\pm j3}{50} = \pm j0.06 \text{ S}$$

The distance between the load and the stub is deter-

$$l_A = \frac{180 - (17.2 - 10)}{720} \lambda = \underline{0.24\lambda}$$

(Exact value = 0.2308λ)

For B,

$$l_B = \frac{180 + 10 + 17}{720} \lambda = \underline{0.2875 \lambda}$$

The length of the stub line is determined as follows.


$$d_{\lambda} = \frac{19}{720} \lambda = \underline{0.0264 \lambda}$$

Exact value = 0.0515λ)

$$d_B = \frac{360 - 19}{720} \lambda = \underbrace{0.4736 \lambda}_{}$$

Exact value = 0.4485λ)
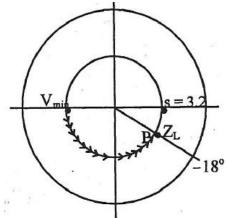
$$\frac{\lambda}{2} = 32 - 12 = 20cm \to \lambda = 40 \text{ cm}$$
$$f = \frac{u}{\lambda} = \frac{3 \times 10^8}{40 \times 10^{-2}} = 0.75 \text{ GHz}$$



$$l = 21 - 12 = 9cm = \frac{9\lambda}{40} \rightarrow \frac{9}{40} \times 720^{\circ} = 162^{\circ}$$

At P,
$$z_L = 2.6 - j1.2$$

$$Z_{\rm L} = z_{\rm L} Z_{\rm o} = 50(2.6 - j1.2) = \underline{130 - j60\Omega}$$

(Exact value = $130.49 - j58.219 \Omega$)